

Anish Sharma

60003220045

IO11

Exp: 6

LDCA

Aim: To design and implement 2-bit magnitude comparator using basic gates.

Apparatus: IC 7408, IC 7486, IC 7432, IC 7404

Theory:


Magnitude comparator is a combinational circuit that compare two number A and B. It determines the relative magnitude according to the comparison. Digital or binary comparators are made up from standard AND, NOR, NOT gates that compare the digital signals present at their input terminals and produce an output depending upon the condition of those inputs.

Identity Comparator -

It is a digital comparator that has three output terminals, one each for $A=B$ either 'HIGH' $A=B$ or 'LOW' $A \neq B$.


Magnitude Comparator -

 A magnitude comparator is a digital comparator that has three output terminals, one each for equality. $A=B$, $A > B$, $A < B$.



* 1-bit magnitude comparator

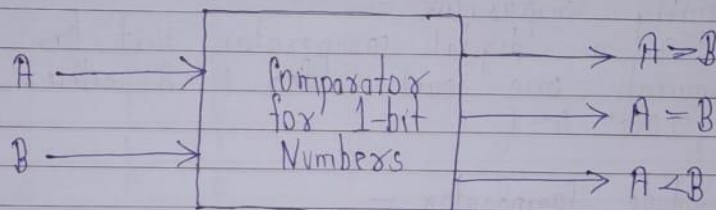A comparator used to compare two bits is called a single bit comparator. It consists of two input each for two single bit numbers and three outputs to generate less than, equal to and greater between two binary numbers.




$$\overline{AB} + A\overline{B} = \overline{AB} + A\overline{B}$$

$$(A + \overline{B}) \cdot (\overline{A} + B) = \overline{AA} + A\overline{B} + \overline{A}B + \overline{BB}$$

$$= \overline{AB} + A\overline{B}$$


* 2 Bit Magnitude Comparators

 

Truth Table :-

A ₁	A ₀	B ₁	B ₀	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

Input		Output		
A	B	$A=B$	$A>B$	$A<B$
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

 

$$\begin{aligned}
 \therefore (A < B) &= A'B \\
 (A = B) &= A'B' + AB = (A \oplus B)' \\
 (A > B) &= AB'
 \end{aligned}$$

Kmap


A\B	00	01	11	10
00				
01	1			
11	1	1		1
10	1	1		

A\B	00	01	11	10
00	1			
01		1		
11			1	
10				1

$$A > B = A_0 \bar{B}_0 \bar{B}_1 + A_1 \bar{B}_1 + A_1 A_0 \bar{B}_0 \quad A = B = (A_0 \oplus B_0) (A_1 \oplus B_1)$$

Logic Diagram:-

2 Bit Magnitude Comparator

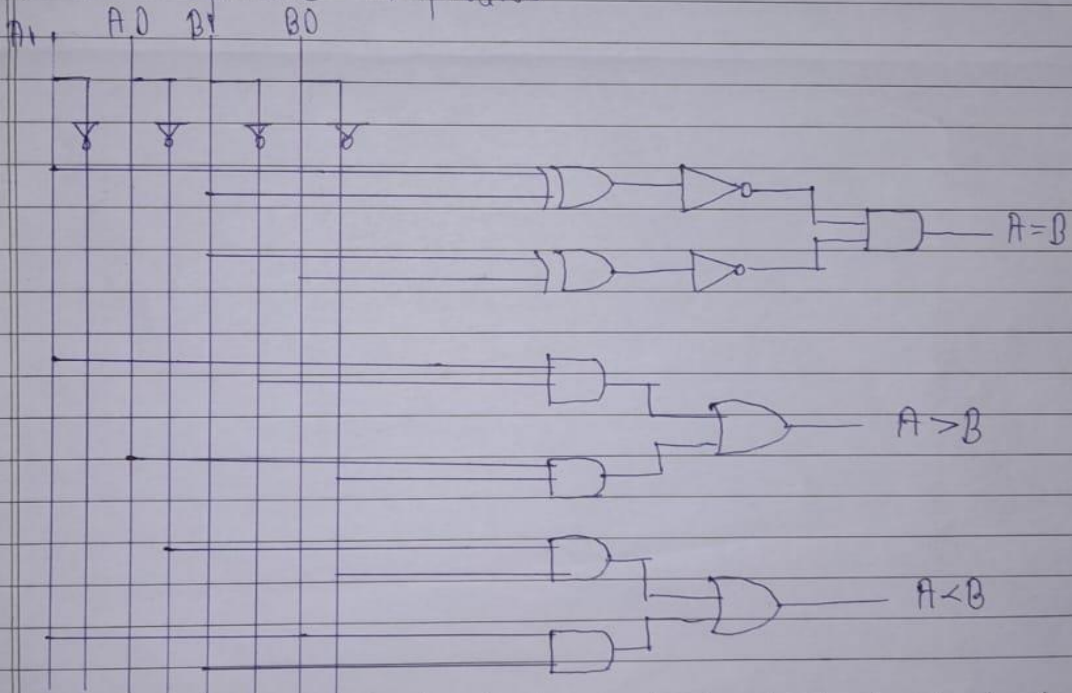

Procedure :-

- (i) Connections are given as per circuit diagram.
- (ii) Logical inputs are given as per circuit diagram.
- (iii) Observe the outputs and verify the truth table.

Conclusion :

I have understood the concept of comparator magnitude with its logical circuit.

