

Anish Sharma

IT1

I011

LDCA

SAP: 60003220045

## Exp 1: Basic Gates

Aim: Study of basic logic Gates

Apparatus: Digital electronics wires, probes, etc.

Component: IC

Theory:


### 1 AND Gate

Truth table:

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Equation:  $Y = A \cdot B$

Symbol:

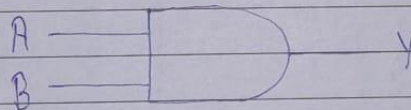

K-map:


B \ A	0	1
0	0	0
1	0	1

## 2. OR Gate

Truth Table :

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Equation :  $Y = A + B$

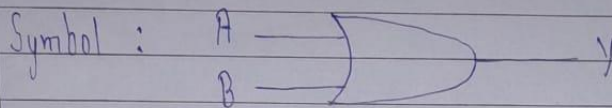

K-map :

B \ A	0	1
0	0	1
1	1	1

## 3. NAND Gate


Truth Table :

A	B	$Y = \overline{A \cdot B}$
1	1	0
1	0	1
0	1	1
0	0	1

Equation :  $Y = \overline{A \cdot B}$

K-map :

B \ A	0	1
0	1	1
1	1	0

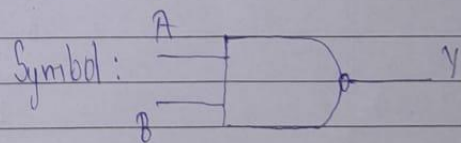


#### 4 NOT - Gate

Truth Table:

A	$Y = \overline{A}$
0	1
1	0

Equation:  $Y = \overline{A}$

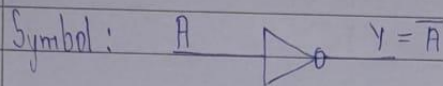


#### 5 NOR Gate

Truth Table:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Equation:  $Y = \overline{A+B}$

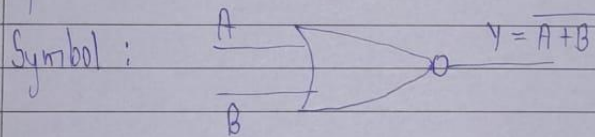

Kmap:


B \ A	0	1
0	1	0
1	0	0

## 6 X-OR Gate

Truth Table :

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Equation :  $Y = A \oplus B$

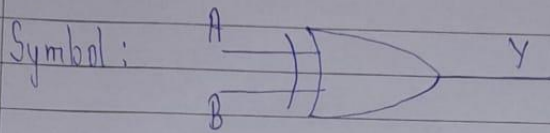


kmap :

B \ A	0	1
0	0	1
1	1	0

## AND Gate

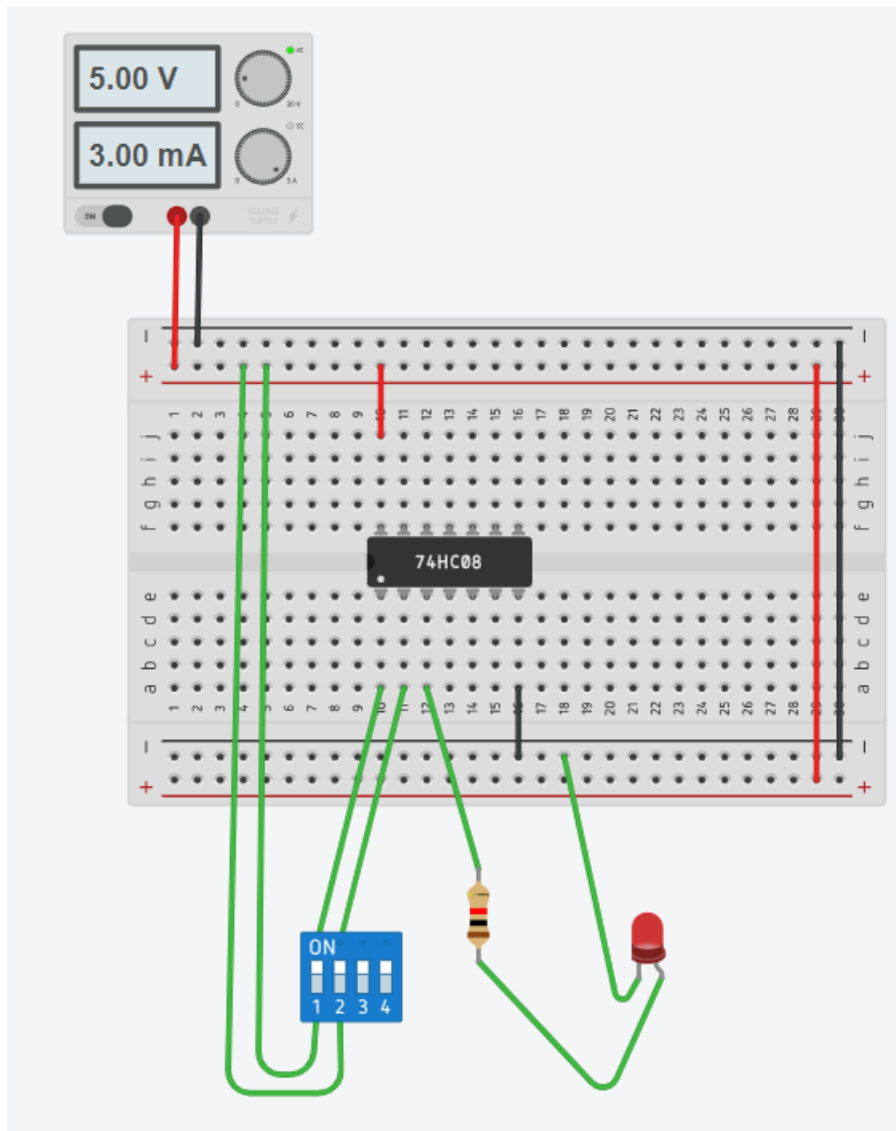


## OR Gate

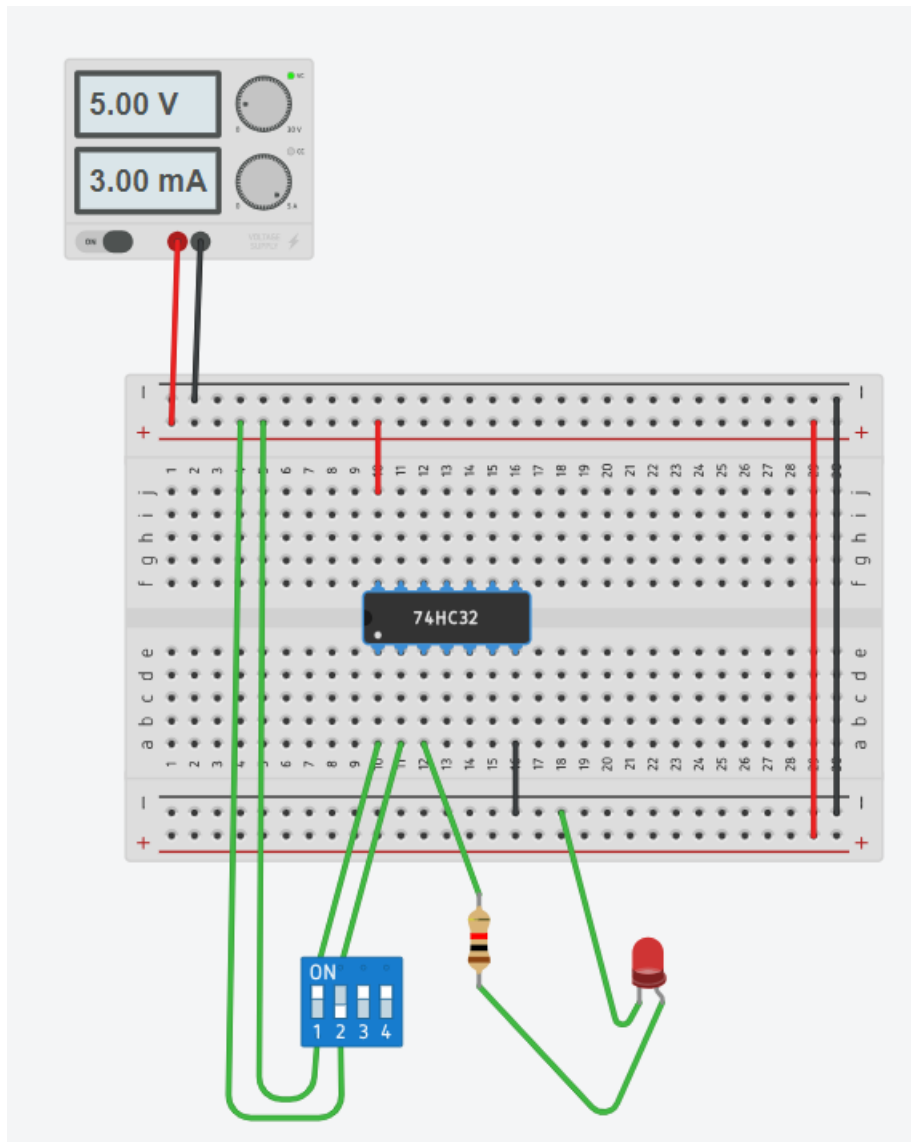




# NOT Gate

Name 3

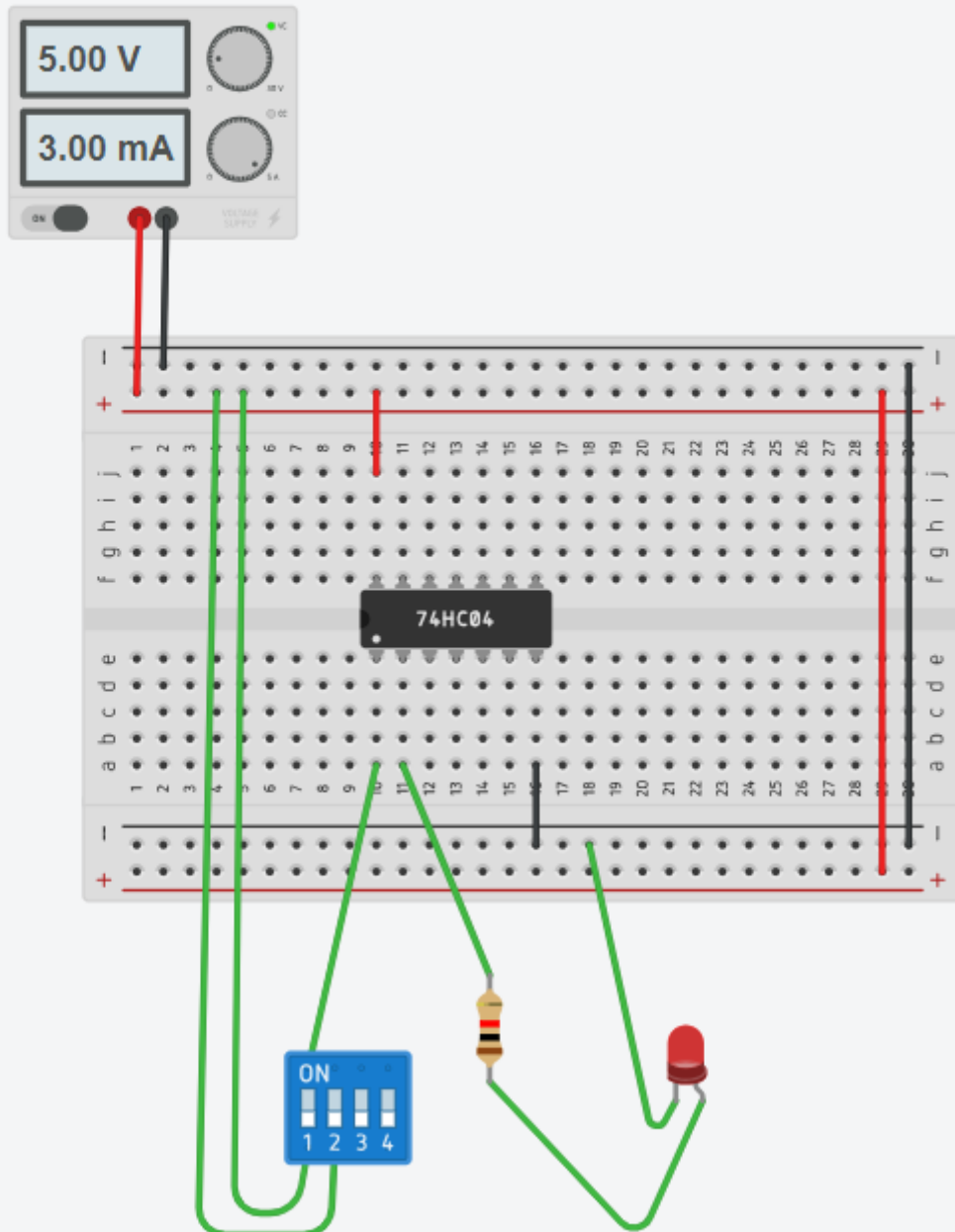


## NAND Gate

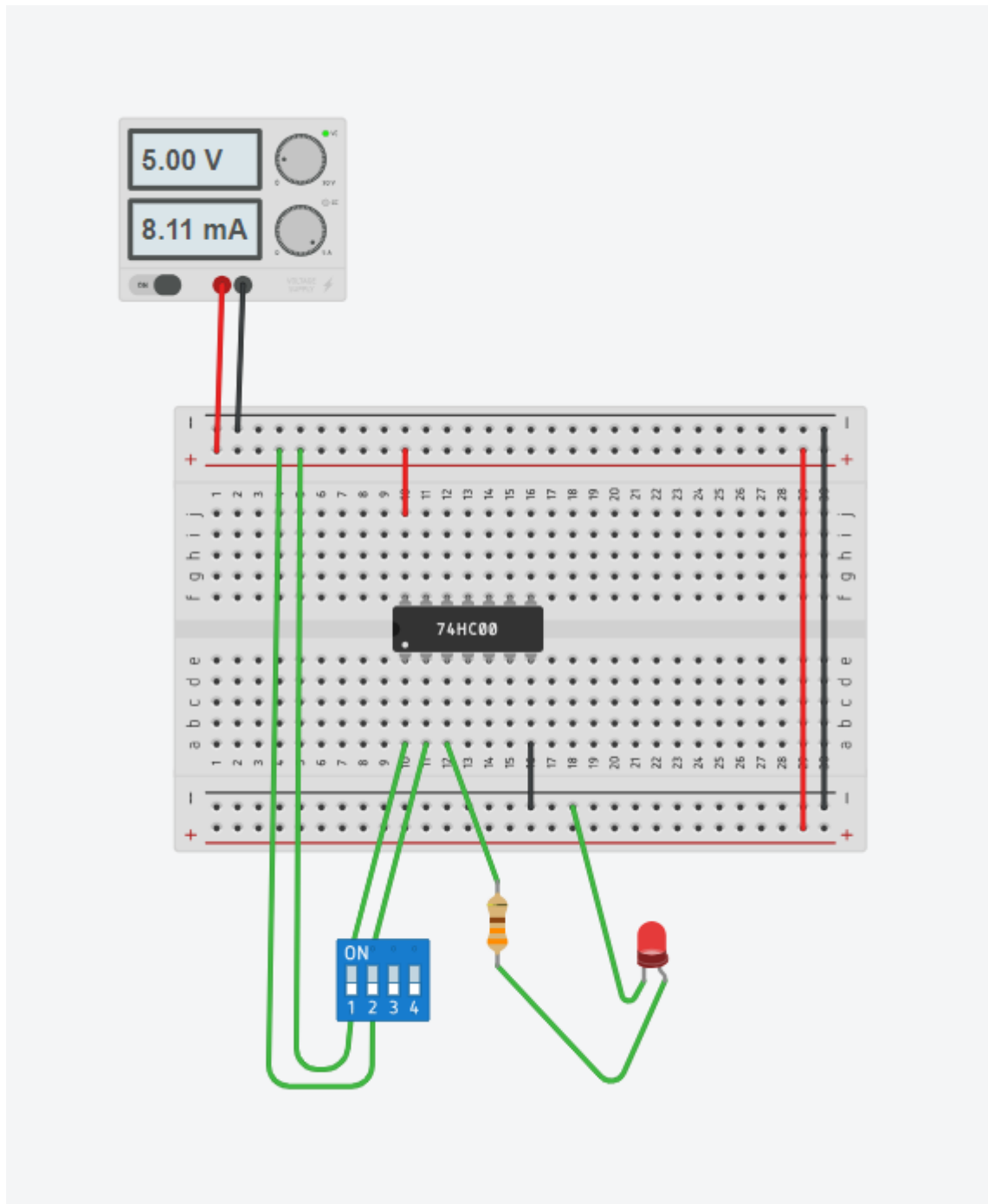



## NOR Gate

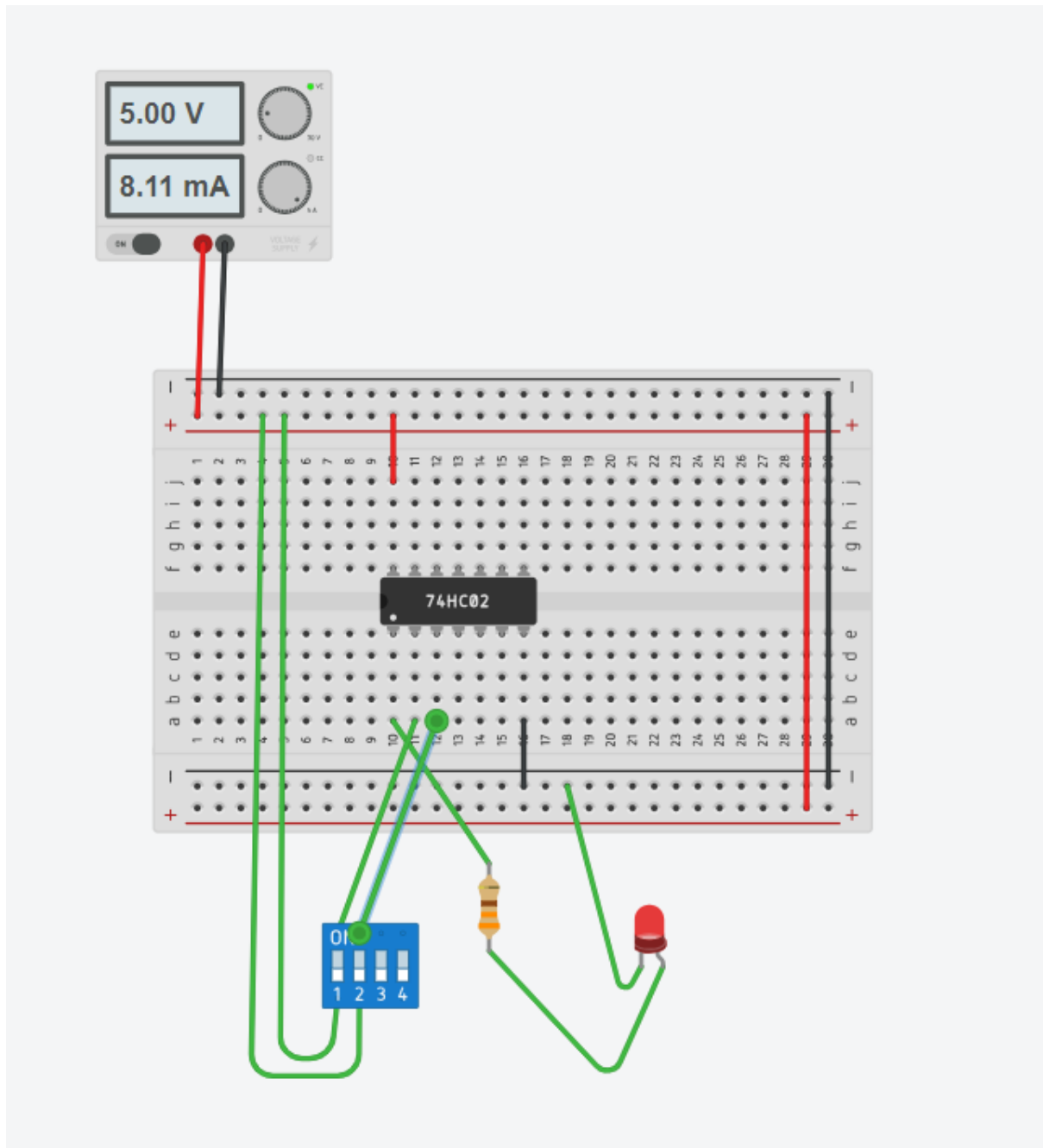

## XOR Gate

