

Exp: 2

LDCA

Aim: Realization of logic gates using NAND and NOR Gates

Components: IC 7400, 7402


Apparatus: Digital trainer, wire, etc

Theory:

The NAND and NOR gates are called as universal gates, because it is possible to implement any Boolean expression with the help of only NAND or NOR gates.


All gates using NAND Gates  $\rightarrow$

1 NOT using NAND

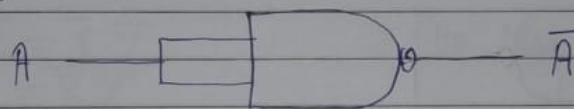

$$\therefore Y = \bar{A}$$


2 AND using NAND

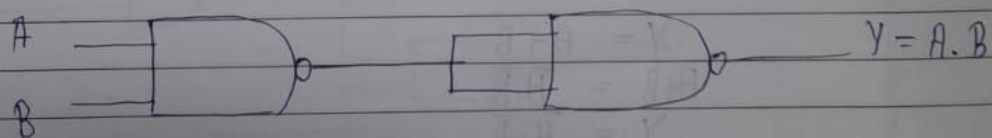

$$Y = \overline{\bar{A} \cdot \bar{B}} \quad \therefore \bar{\bar{A}} = A$$

$$Y = A.B$$

3 OR using NAND

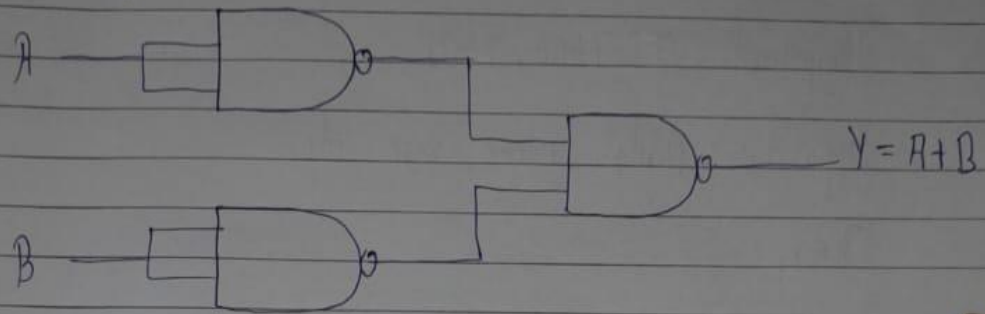


$$Y = \overline{\overline{A+B}}$$

$$\overline{A+B} = \overline{\overline{A} \cdot \overline{B}} \quad \text{(De - Morgan's Theorem)}$$

$$Y = \overline{\overline{A} \cdot \overline{B}}$$

4 NOR using NAND

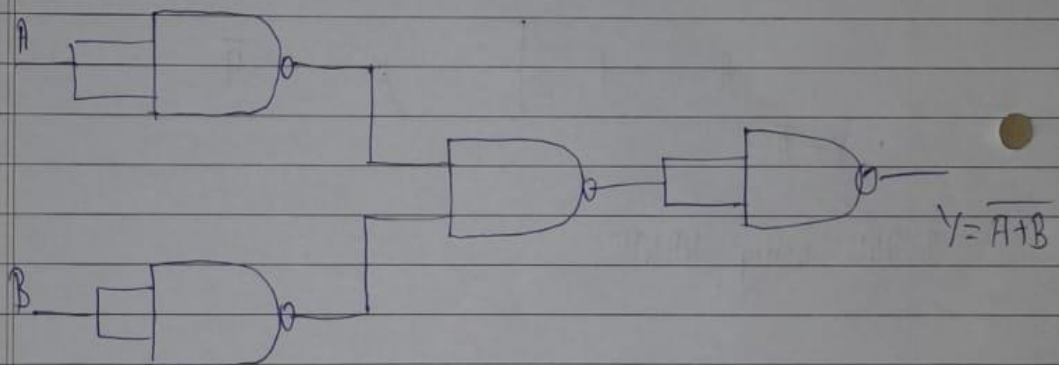


$$Y = \overline{A+B}$$

$$\overline{A+B} = \overline{\overline{A} \cdot \overline{B}}$$

$$Y = \overline{\overline{A} \cdot \overline{B}}$$

$$Y = \overline{\overline{A} \cdot \overline{B}}$$

### 5 EX-OR using NAND

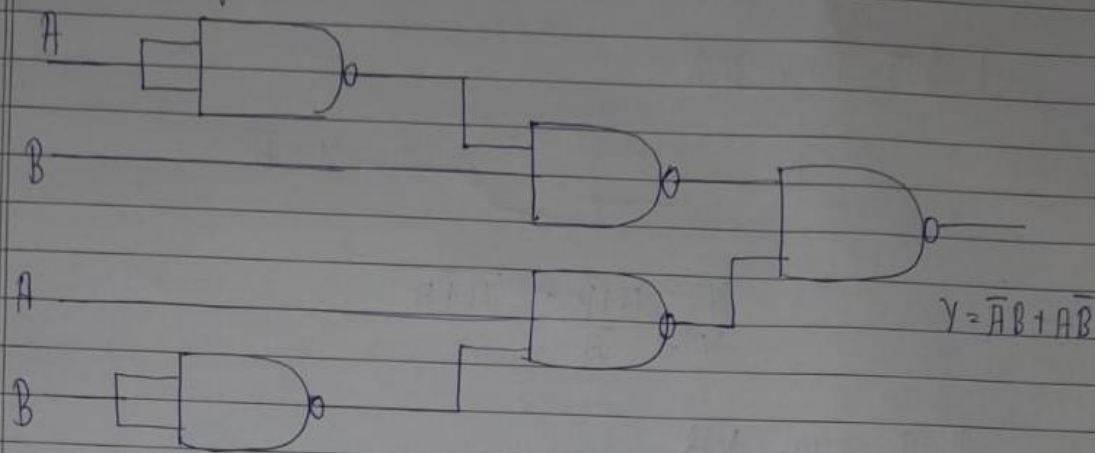

$$Y = A \oplus B = \bar{A} \cdot B + A \cdot \bar{B}$$

$$Y = \overline{\overline{A \cdot B} + \overline{A \cdot B}}$$

$$Y = \overline{X + Z}$$

$$(\bar{A} \cdot B = X, A \cdot \bar{B} = Z)$$


$$\overline{X + Z} = \overline{X} \cdot \overline{Z}$$

$$Y = \overline{X} \cdot \overline{Z}$$

(De Morgan's Theorem)


$$Y = (\overline{A \cdot B}) \cdot (\overline{A \cdot B})$$

### 6 EX-NOR Using NAND

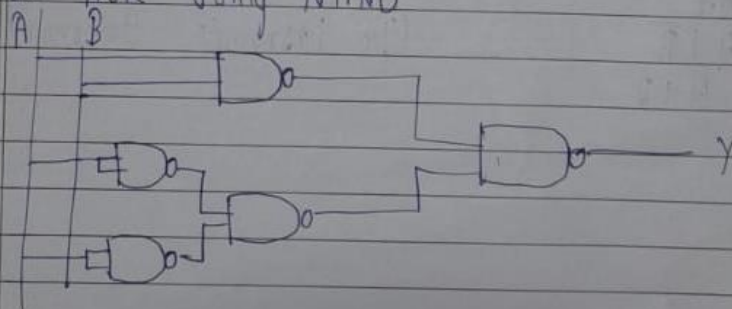


## All gates using NOR Gates

### 1 NOT using NOR

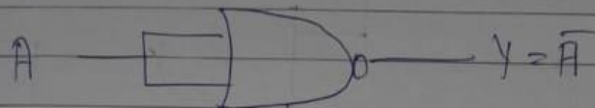

$$Y = \overline{A+B} = \overline{A+A}$$
$$Y = \overline{A}$$

### 2 OR using NOR

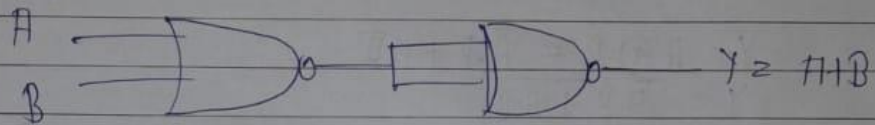

$$Y = \overline{\overline{A+B}}$$


But  $\overline{\overline{A}} = A$

$$Y = A+B$$


### 3 AND using NOR

$$Y = \overline{\overline{A \cdot B}}$$
$$\overline{A \cdot B} = \overline{A+B}$$
$$Y = \overline{\overline{A+B}}$$

(De Morgan's Theorem)

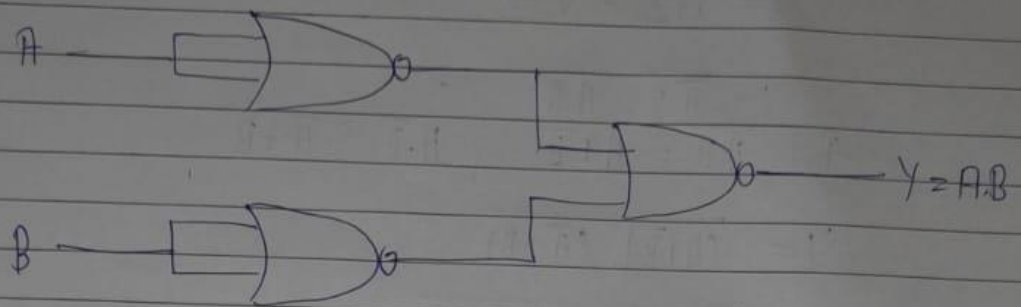

4 NAND using NOR

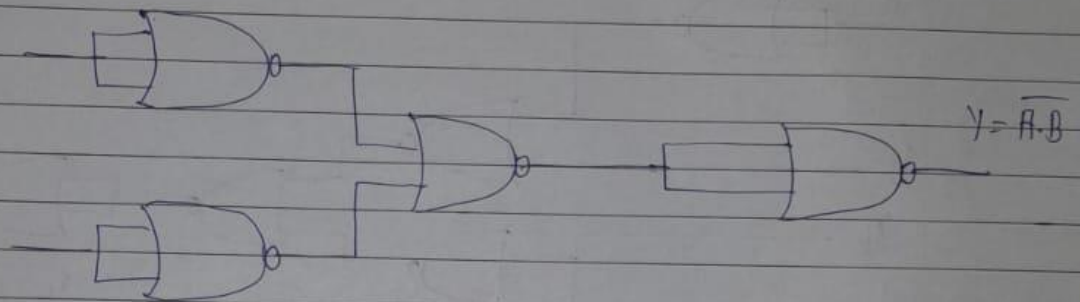

$$Y = \overline{A.B}$$

$$\overline{A.B} = \overline{A} + \overline{B}$$

$$Y = \overline{A} + \overline{B}$$

(De Morgan's)

5 EX-OR using NOR

$$Y = A \oplus B$$

$$Y = \overline{A.B} + A.\overline{B}$$

$$\text{Let } X = \overline{A.B}, \quad Y = A.\overline{B}$$

$$Y = X + Z$$




$$Y = X + Z = \overline{X} \cdot \overline{Z}$$

$$Y = \overline{A \cdot B} \cdot \overline{A \cdot B}$$


$$\text{But } \overline{A \cdot B} = A + \overline{B}, \quad A \cdot \overline{B} = \overline{A + B}$$

$$Y = \overline{(A + \overline{B})} \cdot \overline{(\overline{A} + B)}$$


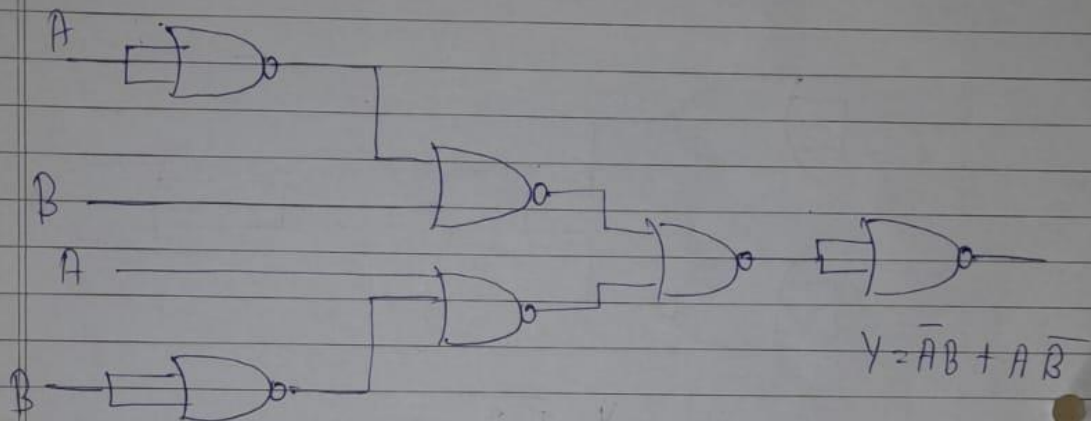
$$Y = \overline{(A + \overline{B})} + \overline{(\overline{A} + B)}$$





6 Ex-NOR using NOR


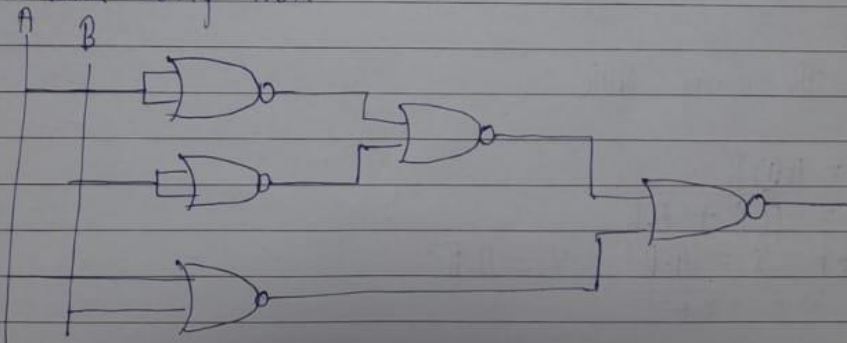


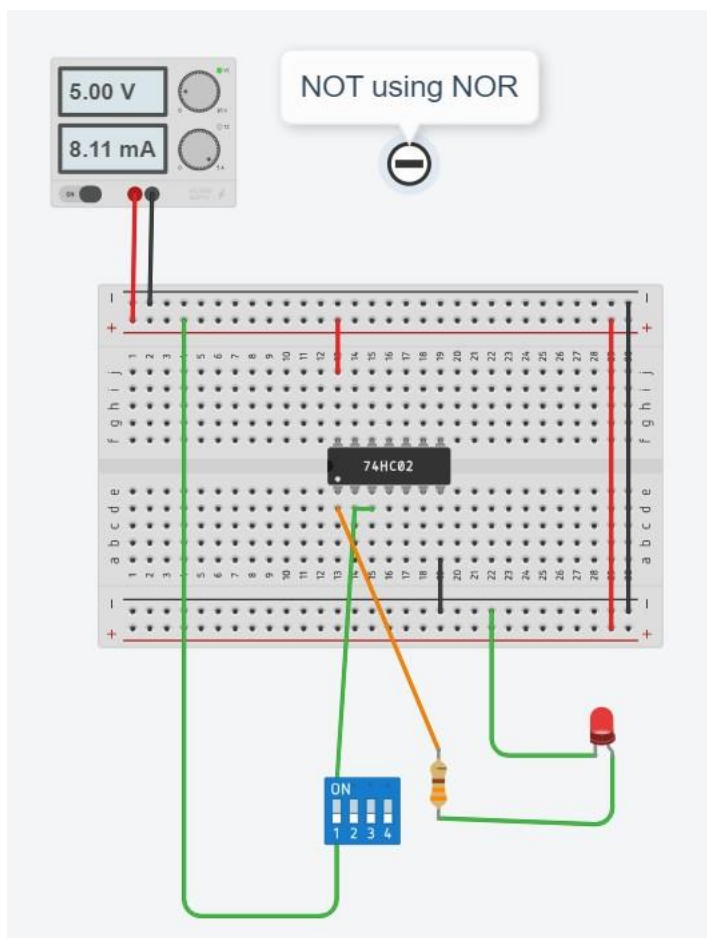
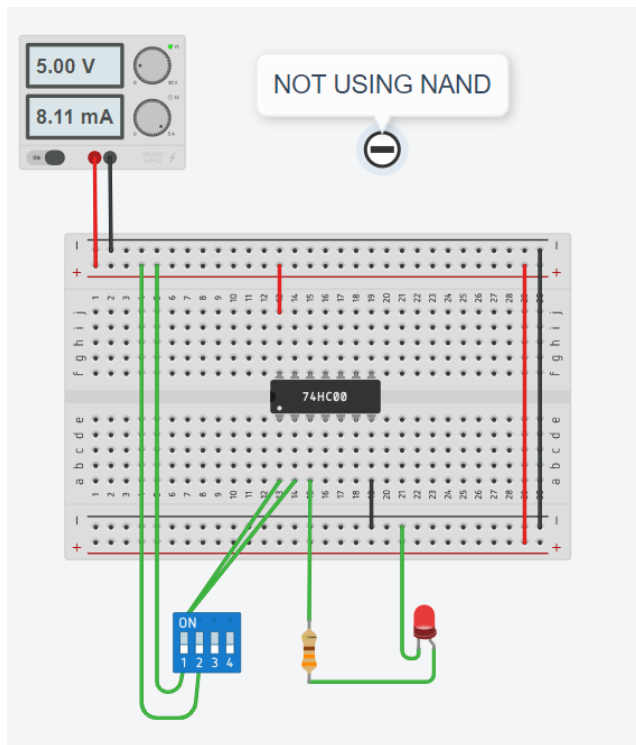
Conclusion: All the gates are realized using NAND and NOR and truth table are verified.




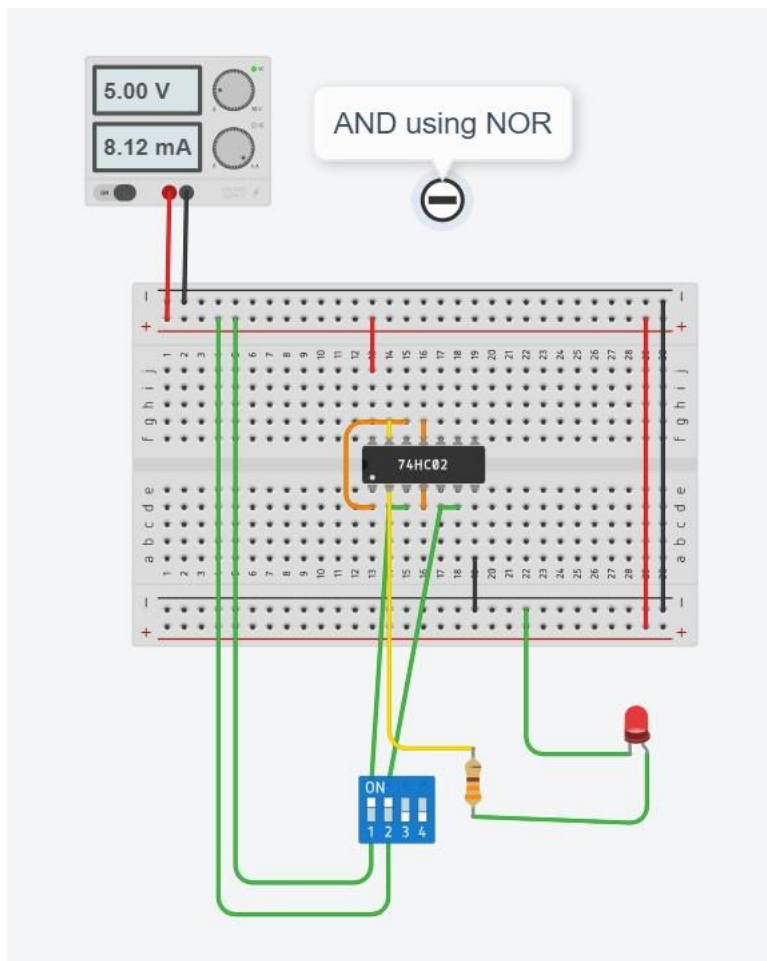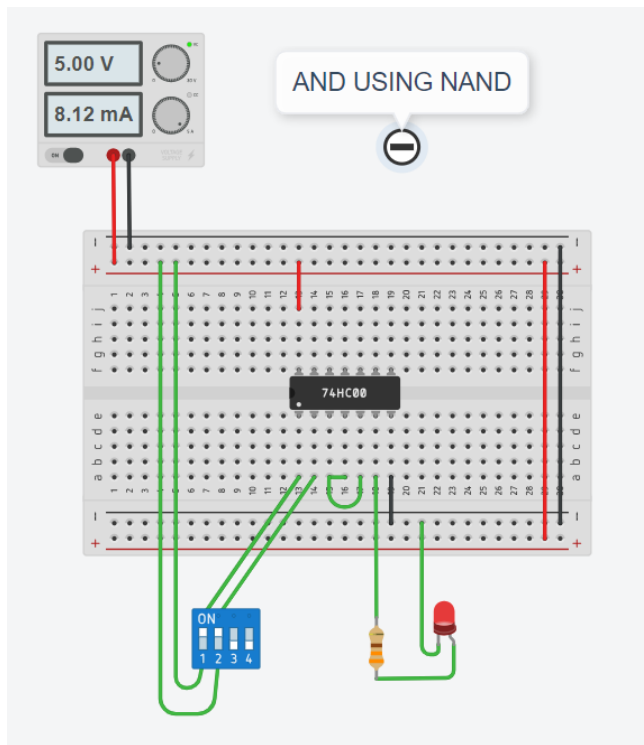




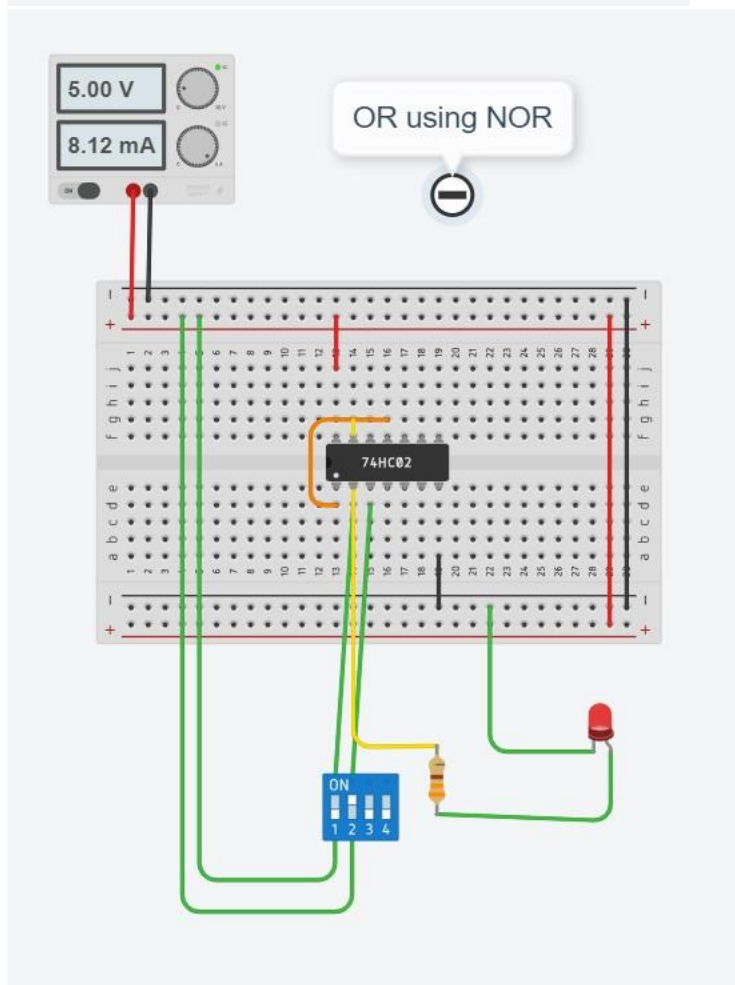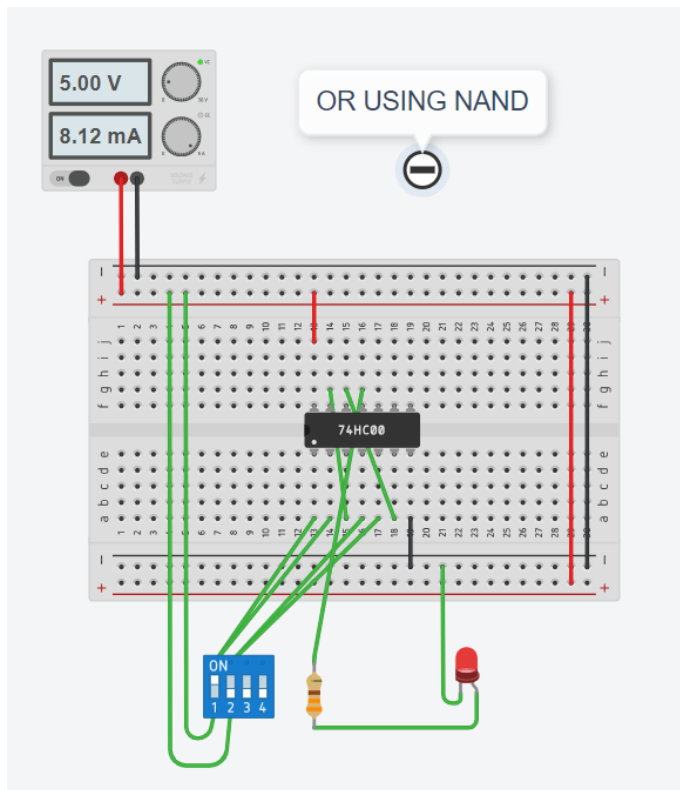

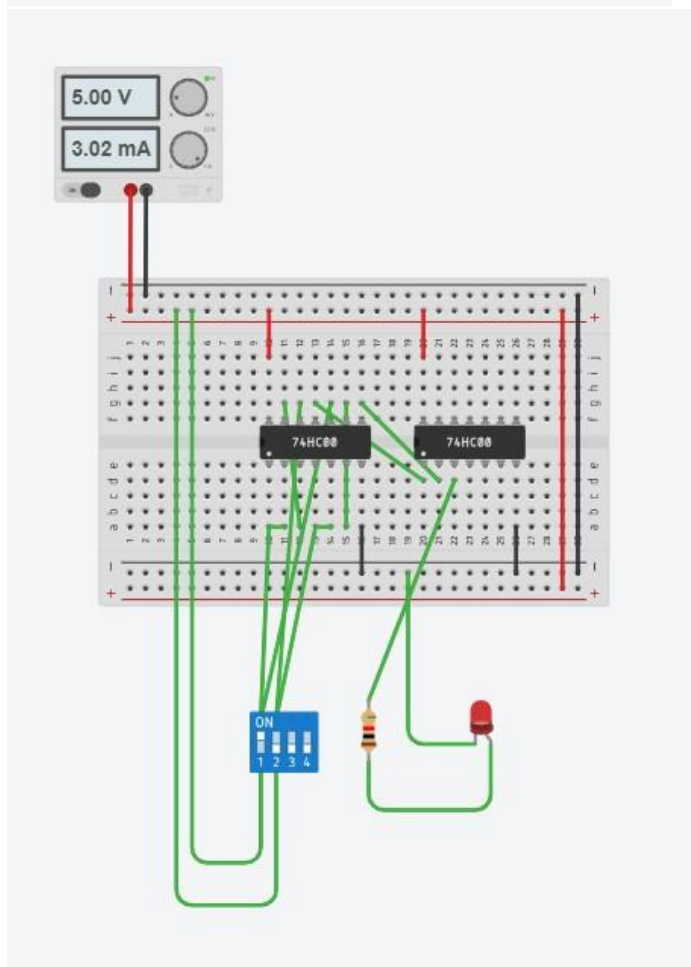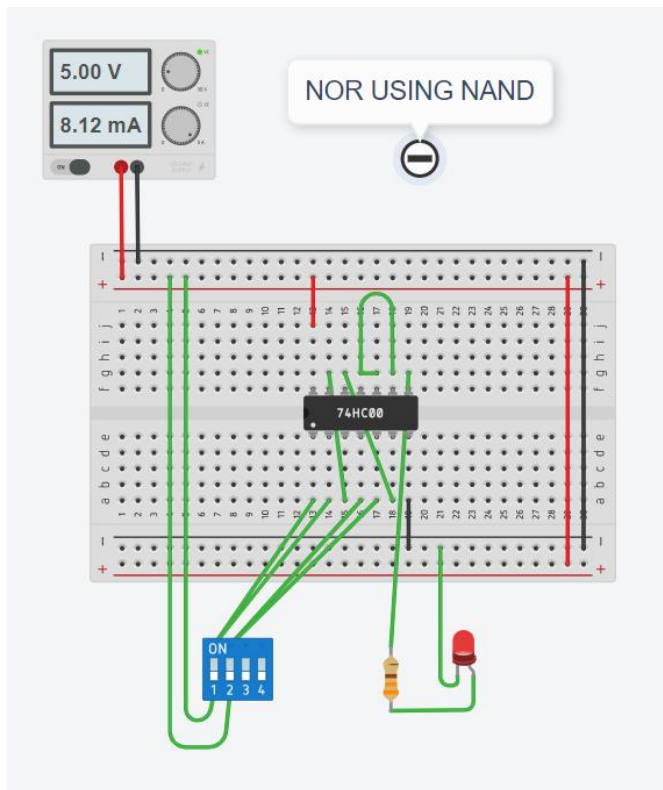

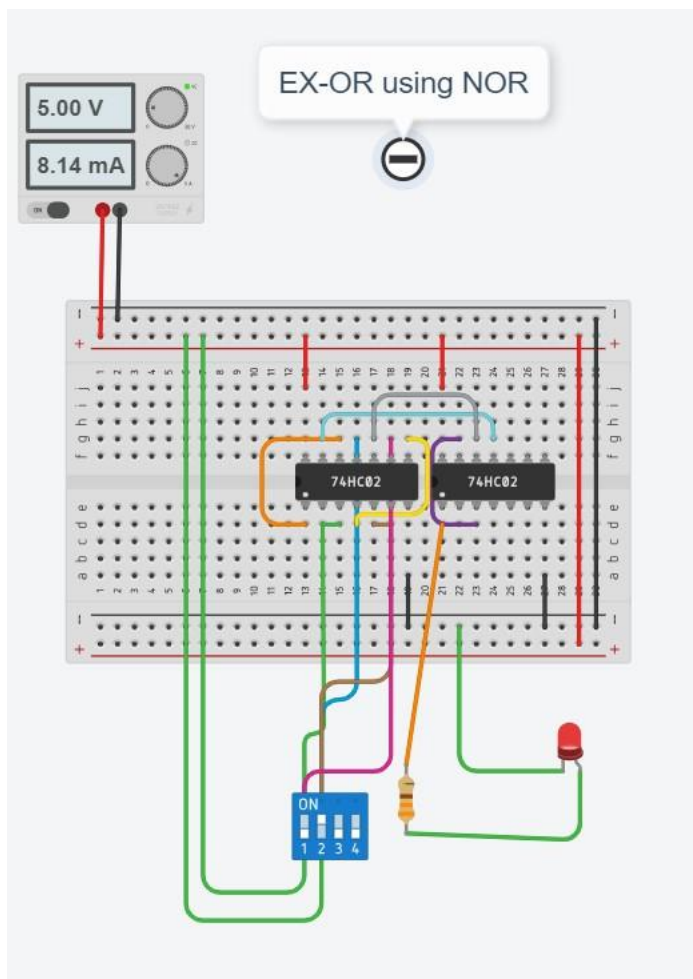

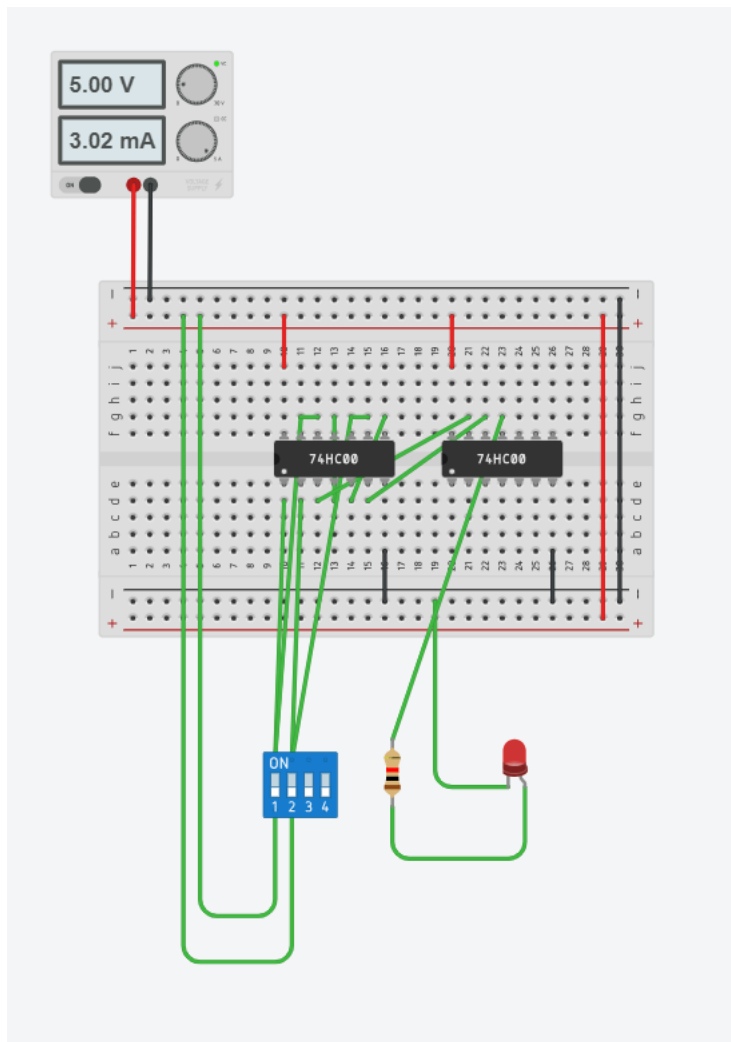


EX-NOR USING NAND

# Ex-NOR using NOR



5.00 V  
8.14 mA

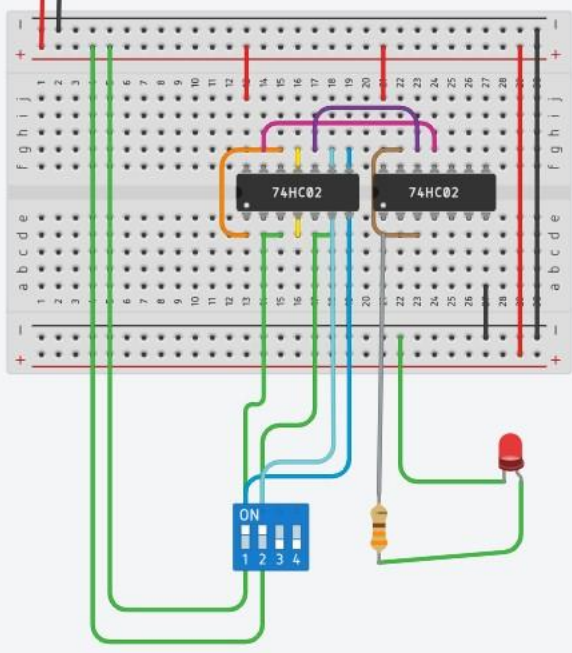





NAND using NOR

